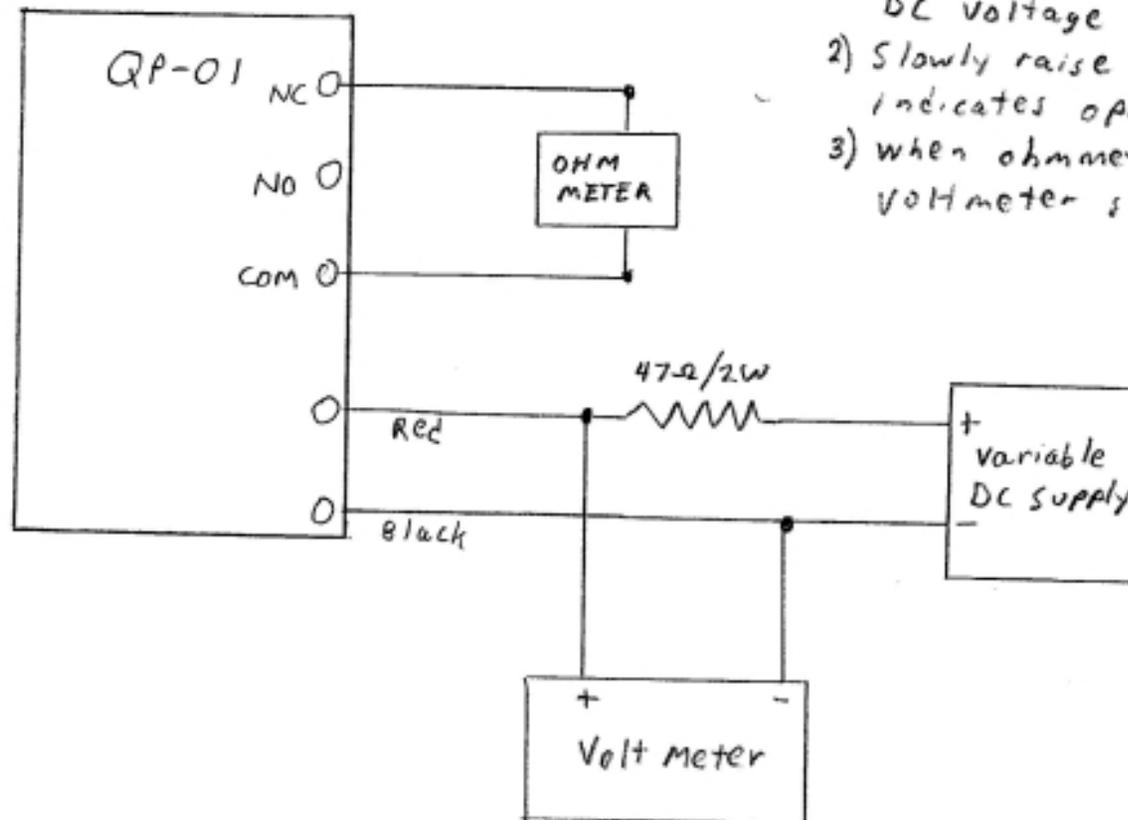


# QP-01 (Sextupole) Test Setup

R. Conte  
6/1/06



- 1) Ohmmeter should read zero ohms with no DC voltage applied.
- 2) Slowly raise DC voltage until ohmmeter indicates open circuit.
- 3) when ohmmeter reads open circuit voltmeter should read approx. 5.15 vdc.